



GOVERNMENT COLLEGE OF ENGINEERING, JALGAON

(An Autonomous Institute of Government of Maharashtra)

National Highway No.6, JALGAON – 425 002

Phone No.: 0257-2281522

Fax No.: 0257-2281319

Website : www.gcoej.ac.in

E-mail : princoej@rediffmail.com



Name of Examination : **Winter 2020** - (Preview)

Course Code & Course Name : **EE201U - Analog Electronics**

Generated At : **19-04-2022 11:04:37**

Maximum Marks : **60**

Duration : **3 Hrs**

[Edit](#) [Print](#) [View Answer Key](#) [Close](#) **Answer Key Submission Type:** Marking scheme with model answers and solutions of numerical

Instructions:

1. All questions are compulsory.
2. Illustrate your answer with suitable figures/sketches wherever necessary.
3. Assume suitable additional data; if required.
4. Use of logarithmic table, drawing instruments and non programmable calculators is allowed.
5. Figures to the right indicate full marks.

1) Que 1 a) is compulsory. Solve any one from sub-question b) and c).

- a) The reverse saturation current of a silicon diode is 3 nA at 27°C. Calculate: [8]
- (i) Reverse saturation current at 82°C.
 - (ii) Forward current at 82°C if forward voltage applied is 0.25 V.
- b) Draw and explain forward and reverse characteristics of Zener Diode. [4]
- c) Give the comparison between Half Wave and Full Wave Rectifier. [4]

2) Que 2 is compulsory.

- a) Draw circuit diagram of BJT common emitter configuration and explain the output characteristics by indicating all the three regions of operation on it. Also, derive the expression for α_{dc} in terms β_{dc} . [8]
- b) What do you mean by oscillator? State and explain Barkhausen criterion with the help of waveforms. [4]

3) Que 3 is compulsory.

- a) Explain following non-idealities in an OP-AMP and specify its ideal value and practical value for IC 741: [8]
- (i) Input Offset Current, (ii) Input Bias Current,
 - (iii) Output Offset Voltage, (iv) Slew Rate.
- b) Draw the circuit diagram of OP-AMP based non-inverting amplifier and calculate the output voltage if $R_1 = 10 \text{ k}\Omega$, $R_F = 20 \text{ k}\Omega$ and V_{in} is 500 mV. [4]

4) Que 4 a) is compulsory. Solve any one from sub-question b) and c).

- a) Draw the circuit diagram of three OP-AMP based Instrumentation amplifier and derive the expression of its output voltage. Also give the applications of Instrumentation Amplifier. [8]
- b) Explain with neat diagram of Analog to Digital Converter. Give the classification and enlist various specifications of it. [4]
- c) Draw the circuit diagram OP-AMP based Wien bridge oscillator and calculate the frequency of oscillations if $R_1 = R_2 = 16 \text{ k}\Omega$ and $C_1 = C_2 = 0.1 \mu\text{F}$. [4]

5) Que 5 is compulsory.

- a) What is PLL? Draw and explain the Frequency Shift Keying (FSK) demodulator using IC 565 PLL. [8]
- b) Draw and explain the working of Zero Crossing Detector (ZCD) with its neat waveforms. [4]

Auto Generated by SsOES v6.2